




Arithmetic Circuits & Multipliers

- Addition, subtraction
 - ripple carry
 - carry bypass
 - carry skip
 - carry lookahead
- Multipliers

Reminder: Lab #3 due tonight!

Signed integers: 2's complement

 

8-bit 2's complement example:

$$11010110 = -2^7 + 2^6 + 2^4 + 2^2 + 2^1 = -128 + 64 + 16 + 4 + 2 = -42$$

If we use a two's complement representation for signed integers, the same binary addition mod 2^n procedure will work for adding positive and negative numbers (don't need separate subtraction rules). The same procedure will also handle unsigned numbers!

By moving the implicit location of "decimal" point, we can represent fractions too:

$$1101.0110 = -2^3 + 2^2 + 2^0 + 2^{-2} + 2^{-3} = -8 + 4 + 1 + 0.25 + 0.125 = -2.625$$

Sign extension


Consider the 8-bit 2's complement representation of:

$$\begin{aligned} 42 &= 00101010 & -5 &= \sim 00000101 + 1 \\ & & &= 11111010 + 1 \\ & & &= 11111011 \end{aligned}$$

What is their 16-bit 2's complement representation?

$$42 = 0000000000101010$$

$$-5 = 1111111111111011$$

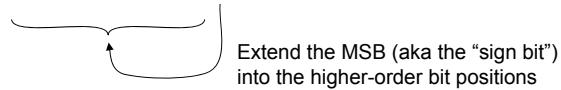


Adder: a circuit that does addition

Here's an example of binary addition as one might do it by "hand":

$$\begin{array}{r} 1101 \\ + 0101 \\ \hline 10010 \end{array}$$


Carries from previous column

 Adding two N-bit numbers produces an (N+1)-bit result




If we build a circuit that implements one column:

 we can quickly build a circuit to add two 4-bit numbers...



"Ripple-carry adder"

“Full Adder” building block

 

The “half adder” circuit has only the A and B inputs




A	B	C	S	CO
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S = A \oplus B \oplus C$$


$$\begin{aligned} CO &= \overline{A}BC + A\overline{B}C + AB\overline{C} + ABC \\ &= (\overline{A} + A)BC + (\overline{B} + B)AC + AB(\overline{C} + C) \\ &= BC + AC + AB \end{aligned}$$

Subtraction: $A - B = A + (-B)$

 Using 2's complement representation: $-B = \sim B + 1$



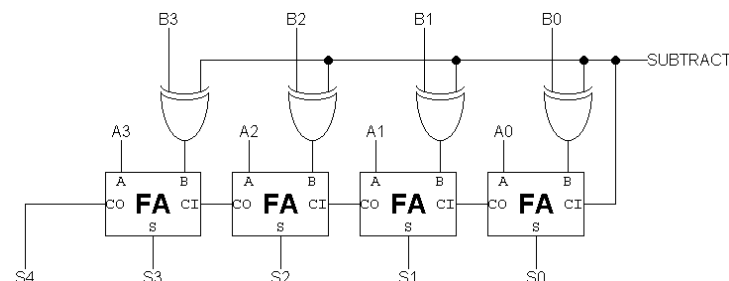So let's build an arithmetic unit that does both addition and subtraction. Operation selected by *control input*:



Condition Codes

Besides the sum, one often wants four other bits of information from an arithmetic unit:

Z (zero): result is = 0 *big NOR gate*

N (negative): result is < 0 *S_{N-1}*

C (carry): indicates an add in the most significant position produced a carry, e.g., 1111 + 0001 *from last FA*

V (overflow): indicates that the answer has too many bits to be represented correctly by the result width, e.g., 0111 + 0111

$$V = A_{N-1}B_{N-1}\overline{S_{N-1}} + \overline{A_{N-1}}\overline{B_{N-1}}S_{N-1}$$

$$V = CO_{N-1} \oplus CIN_{N-1}$$

To compare A and B, perform A-B and use condition codes:

Signed comparison:

LT $N \oplus V$
LE $Z + (N \oplus V)$
EQ Z
NE $\sim Z$
GE $\sim (N \oplus V)$
GT $\sim (Z + (N \oplus V))$

Unsigned comparison:

LTU C
LEU C+Z
GEU $\sim C$
GTU $\sim (C+Z)$

Condition Codes in Verilog

Z (zero): result is = 0

N (negative): result is < 0

C (carry): indicates an add in the most significant position produced a carry, e.g., 1111 + 0001

V (overflow): indicates that the answer has too many bits to be represented correctly by the result width, e.g., 0111 + 0111

```
wire signed [31:0] a,b,s;
wire z,n,v,c;
assign {c,s} = a + b;
assign z = ~|s;
assign n = s[31];
assign v = a[31]^b[31]^s[31]^c;
```

Might be better to use sum-of-products formula for V from previous slide if using LUT implementation (only 3 variables instead of 4).

Modular Arithmetic

The Verilog arithmetic operators (+, -, *) all produce full-precision results, e.g., adding two 8-bit numbers produces a 9-bit result.


In many designs one chooses a “word size” (many computers use 32 or 64 bits) and all arithmetic results are truncated to that number of bits, i.e., arithmetic is performed modulo $2^{\text{word size}}$.

Using a fixed word size can lead to **overflow**, e.g., when the operation produces a result that's too large to fit in the word size. One can

- **Avoid overflow**: choose a sufficiently large word size
- **Detect overflow**: have the hardware remember if an operation produced an overflow - trap or check status at end
- **Embrace overflow**: sometimes this is exactly what you want, e.g., when doing index arithmetic for circular buffers of size 2^N .
- **“Correct” overflow**: replace result with most positive or most negative number as appropriate, aka *saturating arithmetic*. Good for digital signal processing.

Speed: t_{PD} of Ripple-carry Adder

$$C_o = AB + AC_i + BC_i$$

 


Worst-case path: carry propagation from LSB to MSB, e.g., when adding 11...111 to 00...001.

$$t_{PD} = (N-1) * (\underbrace{t_{PD,OR} + t_{PD,AND}}_{CI \text{ to } CO}) + \underbrace{t_{PD,XOR}}_{CI_{N-1} \text{ to } S_{N-1}} \approx \Theta(N)$$

$$t_{adder} = (N-1)t_{carry} + t_{sum}$$


$\Theta(N)$ is read “order N”: means that the latency of our adder grows at worst in proportion to the number of bits in the operands.

How about the t_{PD} of this circuit?

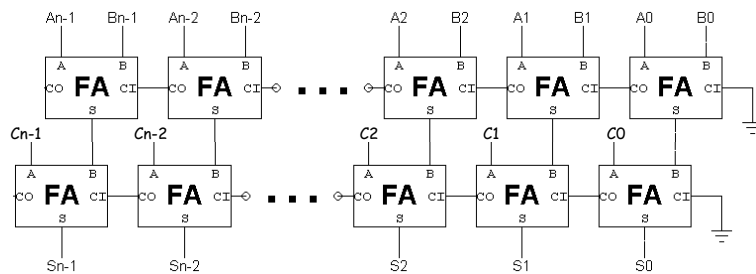

Is the t_{PD} of this circuit = $2 * t_{PD,N-BIT \text{ RIPPLE}}$?

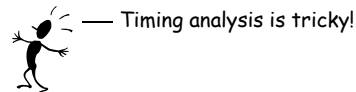
Nope! t_{PD} of this circuit = $t_{PD,N-BIT \text{ RIPPLE}} + t_{PD,FA}$!!!



Alternate Adder Logic Formulation

How to Speed up the Critical (Carry) Path?
(How to Build a Fast Adder?)

A	B	C_i	S	C_o	Carry status
0	0	0	0	0	delete
0	0	1	1	0	delete
0	1	0	1	0	propagate
0	1	1	0	1	propagate
1	0	0	1	0	propagate
1	0	1	0	1	propagate
1	1	0	0	1	generate
1	1	1	1	1	generate

 

Generate (G) = AB
Propagate (P) = A ⊕ B


$$C_o(G, P) = G + PC_i$$

$$S(G, P) = P ⊕ C_i$$

Note: can also use $P = A + B$ for C_o .

Faster carry logic

 Let's see if we can improve the speed by rewriting the equations for C_{OUT} :



$$C_{OUT} = AB + AC_{IN} + BC_{IN}$$

$$= AB + (A + B)C_{IN}$$

$$= G + P C_{IN}$$

generate propagate


where $G = AB$
 $P = A + B$

```


module fa(input a,b,cin, output s,cout);
  wire g = a & b;
  wire p = a ^ b;
  assign s = p ^ cin;
  assign cout = g | (p & cin);
endmodule
    
```

Actually, P is usually defined as $P = A \oplus B$ which won't change C_{OUT} but will allow us to express S as a simple function:
 $S = P \oplus C_{IN}$

Virtex II Adder Implementation

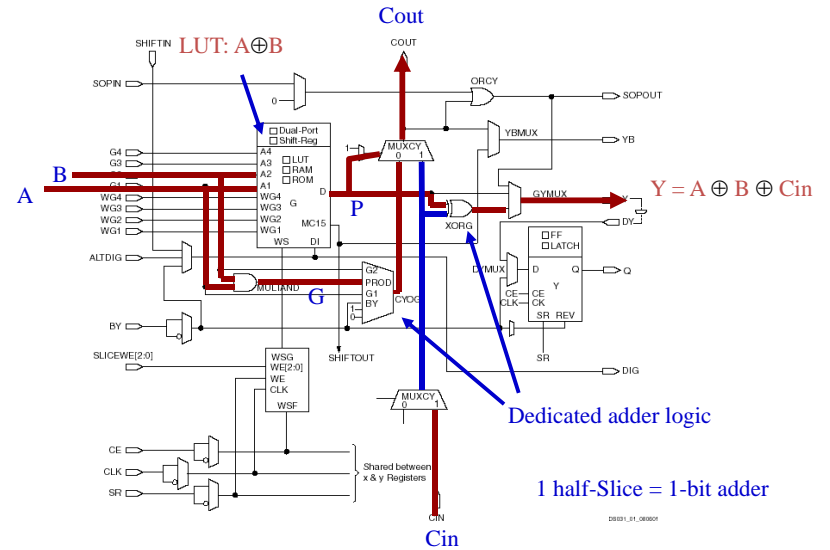

Virtex II Carry Chain

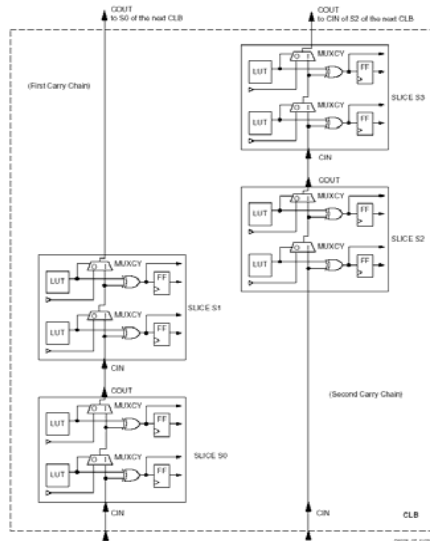

1 CLB = 4 Slices = 2, 4-bit adders
 64-bit Adder: 16 CLBs

$$A[63:0] + B[63:0] \rightarrow Y[63:0]$$

$$A[63:60] \rightarrow Y[64]$$

$$B[63:60] \rightarrow \text{CLB15} \rightarrow Y[63:60]$$

$$A[7:4] \rightarrow \text{CLB1} \rightarrow Y[7:4]$$


$$B[7:4] \rightarrow \text{CLB1} \rightarrow Y[7:4]$$

$$A[3:0] \rightarrow \text{CLB0} \rightarrow Y[3:0]$$


$$B[3:0] \rightarrow \text{CLB0} \rightarrow Y[3:0]$$

CLBs must be in same column

Carry Bypass Adder

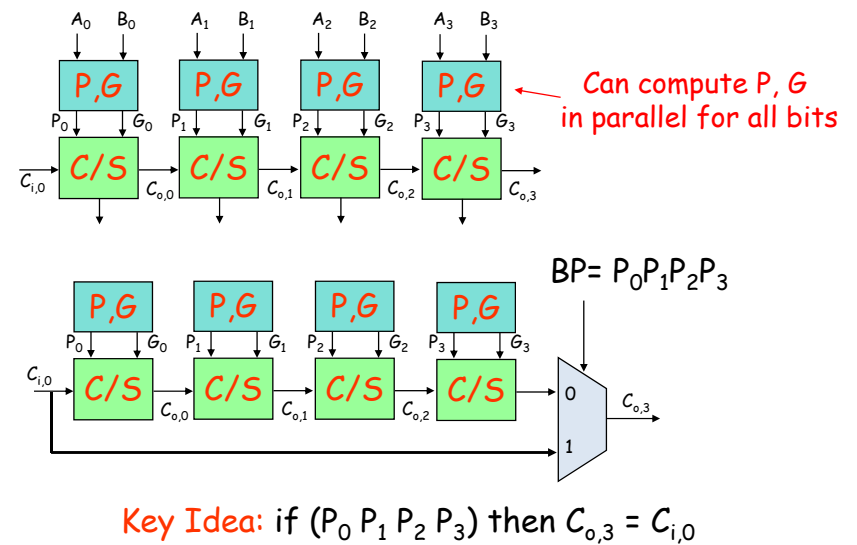


16-bit Carry Bypass Adder

 

What is the worst case propagation delay for the 16-bit adder?

Assume the following for delay each gate:
 P, G from A, B: 1 delay unit
 P, G, C_i to C_o or Sum for a C/S: 1 delay unit
 2:1 mux delay: 1 delay unit

Critical Path Analysis

 

For the second stage, is the critical path:


BP2 = 0 or BP2 = 1 ?

Message: Timing analysis is very tricky - Must carefully consider data dependencies for false paths

Carry Bypass vs Ripple Carry

Ripple Carry: $t_{adder} = (N-1) t_{carry} + t_{sum}$

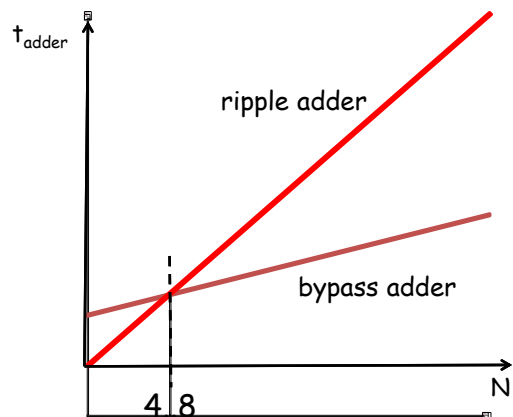Carry Bypass: $t_{adder} = 2(M-1) t_{carry} + t_{sum} + (N/M-1) t_{bypass}$



M = bypass word size
 N = number of bits being added

Carry Lookahead Adder (CLA)

Recall that $C_{OUT} = G + P C_{IN}$ where $G = A \& B$ and $P = A \wedge B$


For adding two N-bit numbers:

$$\begin{aligned}
 C_N &= G_{N-1} + P_{N-1} C_{N-1} \\
 &= G_{N-1} + P_{N-1} G_{N-2} + P_{N-1} P_{N-2} C_{N-2} \\
 &= G_{N-1} + P_{N-1} G_{N-2} + P_{N-1} P_{N-2} G_{N-3} + \dots + P_{N-1} \dots P_0 C_{IN}
 \end{aligned}$$


C_N in only 3 gate delays* :
 1 for P/G generation, 1 for ANDs, 1 for final OR
 *assuming gates with N inputs

Idea: pre-compute all carry bits as f(Gs,Ps,C_{IN})

Carry Lookahead Circuits

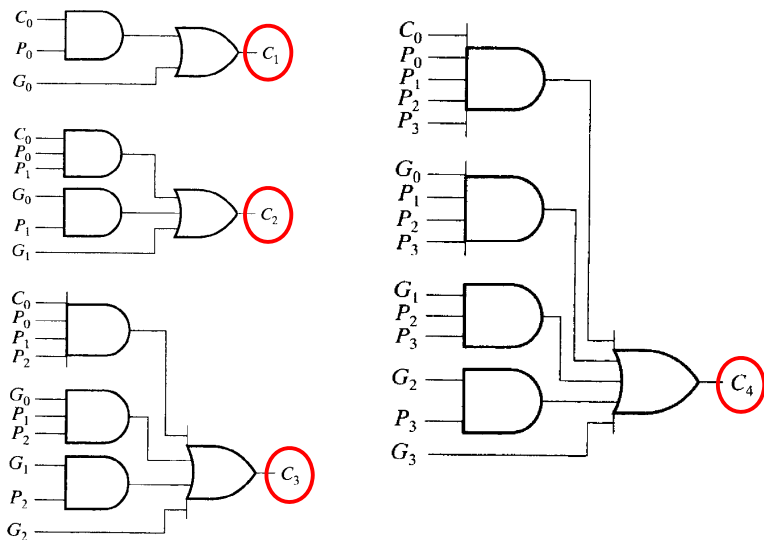

The 74182 Carry Lookahead Unit

 

- high speed carry lookahead generator
- used with 74181 to extend carry lookahead beyond 4 bits
- correctly handles the carry polarity of the 181

Active low example:

$$C_{n+x} = \overline{\overline{G_0 P_0} + \overline{G_0 C_n}} = \overline{G_0 P_0 G_0 C_n} = (G_0 + P_0)(G_0 + C_n) = G_0 + P_0 C_n$$

$$C_4 = G_{3:0} + P_{3:0} C_n$$

$$C_{n+y} = C_8 = G_{7:4} + P_{7:4} G_{3:0} + P_{7:4} P_{3:0} C_{1:0} = G_{7:0} + P_{7:0} C_n$$

$$C_{n+z} = C_{12} = G_{11:8} + P_{11:8} G_{7:4} + P_{11:8} P_{7:4} G_{3:0} + P_{11:8} P_{7:4} P_{3:0} C_n = G_{11:0} + P_{11:0} C_n$$

Block Generate and Propagate

G and P can be computed for groups of bits (instead of just for individual bits). This allows us to choose the maximum fan-in we want for our logic gates and then build a hierarchical carry chain using these equations:


$$C_{J+1} = G_{IJ} + P_{IJ} C_I$$

$$G_{IK} = G_{J+1,K} + P_{J+1,K} G_{IJ}$$

$$P_{IK} = P_{IJ} P_{J+1,K}$$


“generate a carry from bits I thru K if it is generated in the high-order (J+1,K) part of the block or if it is generated in the low-order (I,J) part of the block and then propagated thru the high part”

where $I < J$ and $J+1 < K$

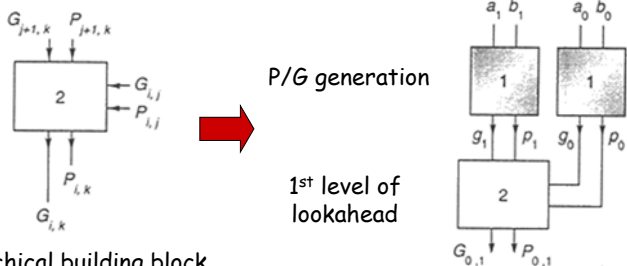


Hierarchical building block

8-bit CLA (P/G generation)

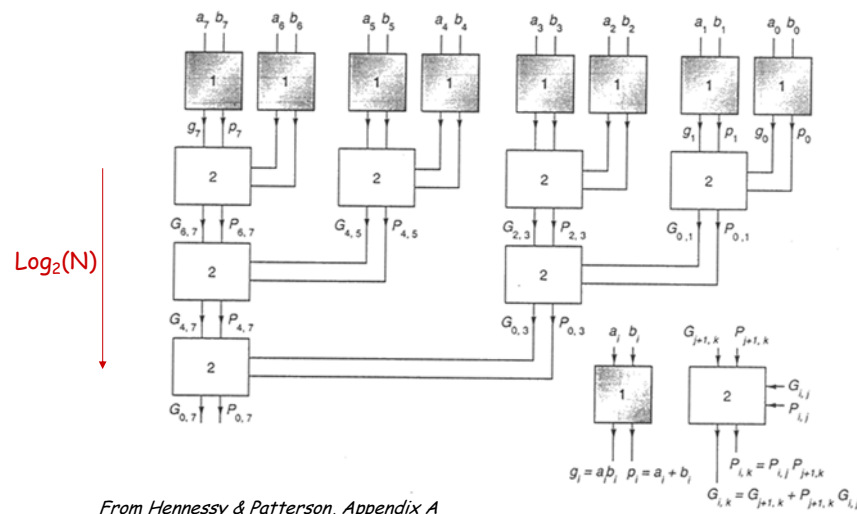


From Hennessy & Patterson, Appendix A


8-bit CLA (carry generation)

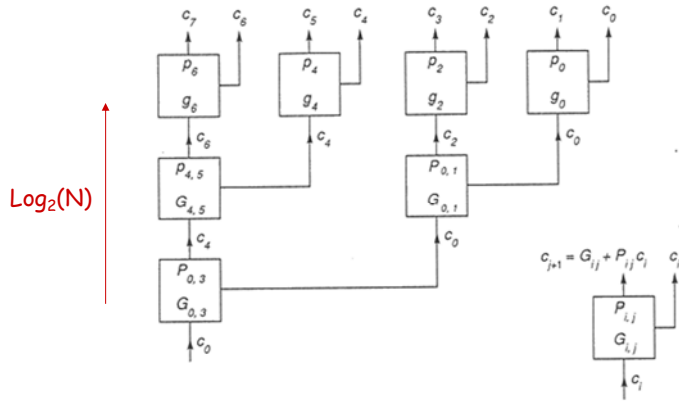

8-bit CLA (complete)

 

Unsigned Multiplication

 


AB_i called a "partial product" $\rightarrow A_3B_0 \ A_2B_0 \ A_1B_0 \ A_0B_0$

Multiplying N-bit number by M-bit number gives (N+M)-bit result

Easy part: forming partial products
 (just an AND gate since B_i is either 0 or 1)
 Hard part: adding M N-bit partial products

Combinational Multiplier (unsigned)


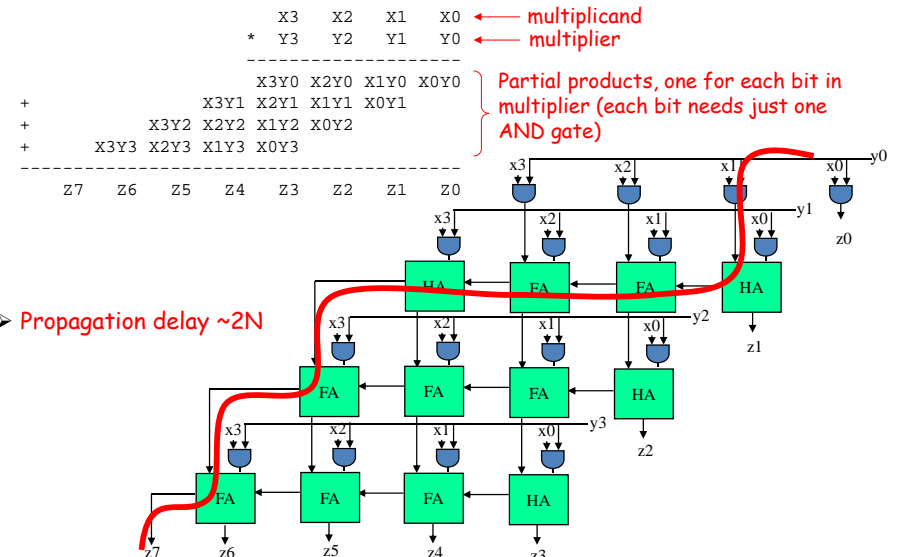


Propagation delay $\sim 2N$

Combinational Multiplier (signed!)

$$\begin{array}{r}
 X3 \\
 * Y3 \\
 \hline
 X3Y0 \\
 + X3Y1 \\
 + X3Y2 \\
 - X3Y3 \\
 \hline

 \end{array}$$

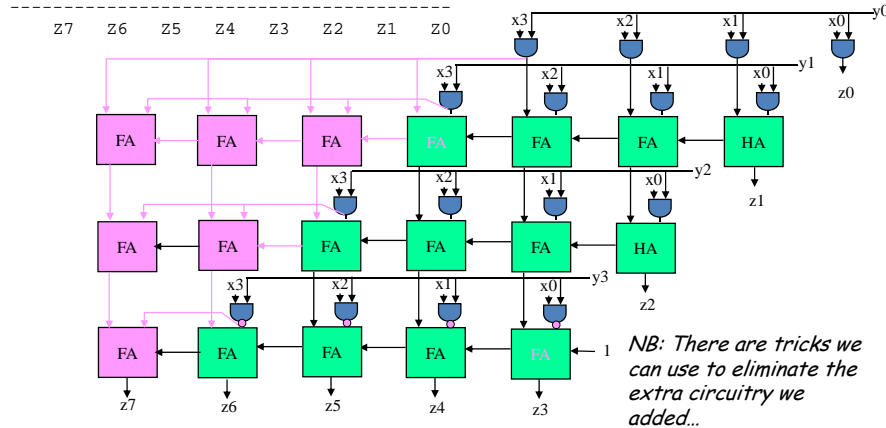 

2's Complement Multiplication (Baugh-Wooley)

Step 1: two's complement operands so high order bit is -2^{N-1} . Must sign extend partial products and **subtract** the last one

$$\begin{array}{r}
 X3 \\
 * Y3 \\
 \hline
 X3Y0 \\
 + X3Y1 \\
 + X3Y2 \\
 - X3Y3 \\
 \hline

 \end{array}$$

Step 2: don't want all those extra additions, so add a carefully chosen constant, remembering to subtract it at the end. Convert subtraction into add of (complement + 1).

$$\begin{array}{r}
 X3Y0 \\
 + \\
 + X3Y1 \\
 + \\
 + X3Y2 \\
 + \\
 + X3Y3 \\
 + \\
 - \\
 \hline

 \end{array}$$

$-B = \sim B + 1$

Step 3: add the ones to the partial products and propagate the carries. All the sign extension bits go away!

$$\begin{array}{r}
 \\
 + \\
 + \\
 + X3Y3 \\
 \hline

 \end{array}$$

Step 4: finish computing the constants...

$$\begin{array}{r}
 \\
 + \\
 + \\
 + X3Y3 \\
 + \\
 \hline

 \end{array}$$

Result: multiplying 2's complement operands takes just about same amount of hardware as multiplying unsigned operands!

Baugh Wooley Formulation -The Math

no insight required

Assuming X and Y are 4-bit two's complement numbers:

$$X = -2^3x_3 + \sum_{i=0}^2 x_i 2^i \quad Y = -2^3y_3 + \sum_{i=0}^2 y_i 2^i$$

The product of X and Y is:

$$XY = x_3y_32^6 - \sum_{i=0}^2 x_iy_32^{i+3} - \sum_{j=0}^2 x_3y_j2^{j+3} + \sum_{i=0}^2 \sum_{j=0}^2 x_iy_j2^{i+j}$$

For two's complement, the following is true:

$$-\sum_{i=0}^2 x_i 2^i = -2^4 + \sum_{i=0}^2 x_i 2^{i+4} - 1$$


The product then becomes:

$$\begin{aligned}
 XY &= x_3y_32^6 + \sum_{i=0}^2 \overline{x_iy_3}2^{i+3} + 2^3 - 2^6 + \sum_{j=0}^2 \overline{x_3y_j}2^{j+3} + 2^3 - 2^6 + \sum_{i=0}^2 \sum_{j=0}^2 x_iy_j2^{i+j} \\
 &= x_3y_32^6 + \sum_{i=0}^2 \overline{x_iy_3}2^{i+3} + \sum_{j=0}^2 \overline{x_3y_j}2^{j+3} + \sum_{i=0}^2 \sum_{j=0}^2 x_iy_j2^{i+j} + 2^4 - 2^7 \\
 &= -2^7 + x_3y_32^6 + \overline{(x_2y_3 + x_3y_2)}2^5 + \overline{(x_1y_3 + x_3y_1 + x_2y_2 + 1)}2^4 \\
 &\quad + \overline{(x_0y_3 + x_3y_0 + x_1y_2 + x_2y_1)}2^3 + (x_0y_2 + x_1y_1 + x_2y_0)2^2 + \\
 &\quad + (x_0y_1 + x_1y_0)2^1 + (x_0y_0)2^0
 \end{aligned}$$

2's Complement Multiplication

$$\begin{array}{r}
 \\
 + \\
 + \\
 + X3Y3 \\
 + \\
 \hline

 \end{array}$$

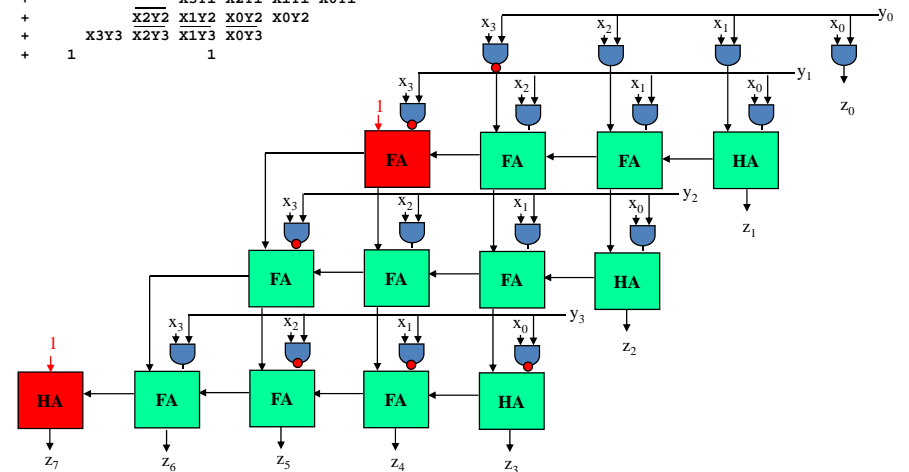

Multiplication in Verilog

You can use the "*" operator to multiply two numbers:

```
wire [9:0] a,b;
wire [19:0] result = a*b; // unsigned multiplication!
```

If you want Verilog to treat your operands as signed two's complement numbers, add the keyword `signed` to your `wire` or `reg` declaration:


```
wire signed [9:0] a,b;
wire signed [19:0] result = a*b; // signed multiplication!
```

Remember: unlike addition and subtraction, you need different circuitry if your multiplication operands are signed vs. unsigned. Same is true of the `>>>` (arithmetic right shift) operator. To get signed operations all operands must be signed.


To make a signed constant: `10'sh37C`

Multiplication on the FPGA

 Hardware multiplier block: two 18-bit two's complement (signed) operands




 In the XC2V6000: 6 columns of mults, 24 in each column = 144 mults



Sequential Multiplier

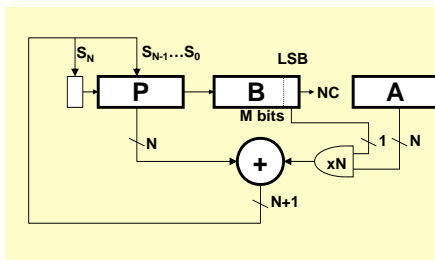Assume the multiplicand (A) has N bits and the multiplier (B) has M bits. If we only want to invest in a single N-bit adder, we can build a sequential circuit that processes a single partial product at a time and then cycle the circuit M times:




Init: $P \leftarrow 0$, load A and B

```
Repeat M times {
  P ← P + (BLSB==1 ? A : 0)
  shift P/B right one bit
}
```

Done: (N+M)-bit result in P/B


Bit-Serial Multiplication

 

```
Init: P = 0; Load A,B
Repeat M times {
  Repeat N times {
    shift A,P:
    Amsb = Alsb
    Pmsb = Plsb + Alsb*Blsb + C/O
  }
  shift P,B: Pmsb = C, Bmsb = Plsb
}
```

(N+M)-bit result in P/B


Combinational Multiplier (unsigned)

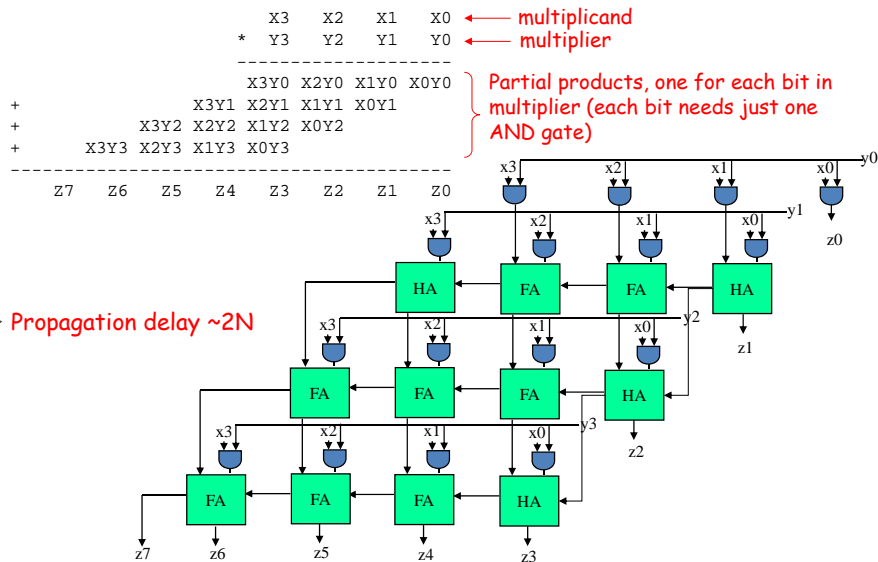

Useful building block: Carry-Save Adder

Good for pipelining: delay through each partial product (except the last) is just $t_{PD,AND} + t_{PD,FA}$.

No carry propagation time!

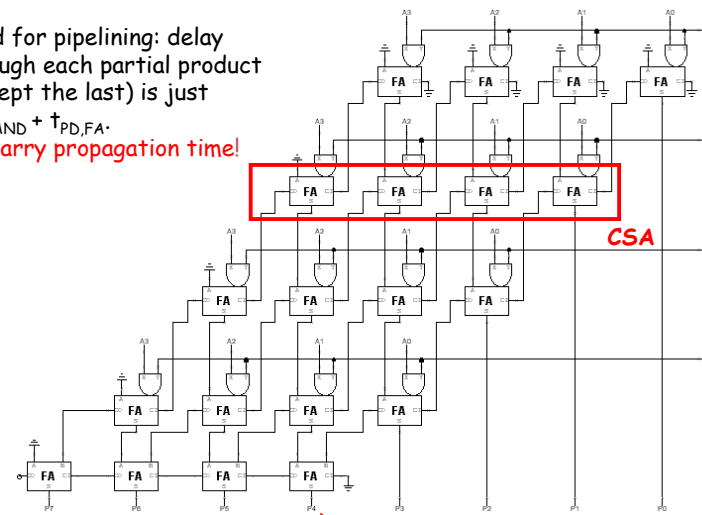


Wallace Tree Multiplier

This is called a 3:2 counter by multiplier hackers: counts number of 1's on the 3 inputs, outputs 2-bit result.

Wallace Tree:
Combine groups of three bits at a time

Higher fan-in adders can be used to further reduce delays for large M.

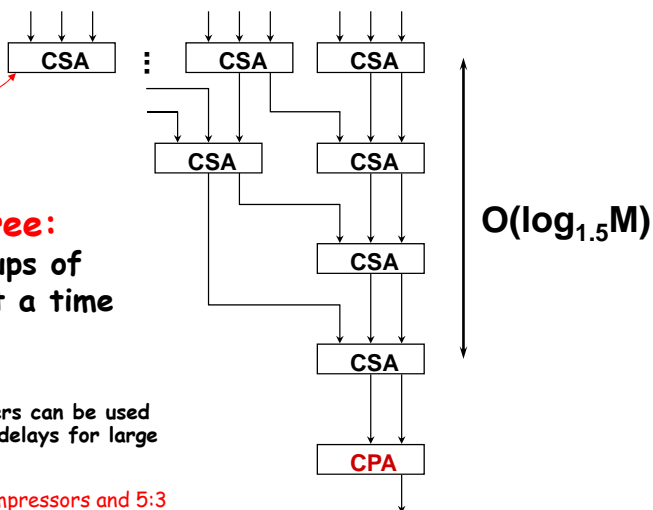4:2 compressors and 5:3 counters are popular building blocks.



Wallace Tree * Four Bit Multiplier

 


Figure 11-35 Wallace tree for four-bit multiplier.

*Digital Integrated Circuits
J Rabaey, A Chandrakasan, B Nikolic

Multiplication by a constant


- If one of the operands is a constant, make it the multiplier (B in the earlier examples). For each "1" bit in the constant we get a partial product (PP) - may be noticeably fewer PPs than in the general case.
 - For example, in general multiplying two 4-bit operands generates four PPs (3 rows of full adders). If the multiplier is say, 12 (4'b1100), then there are only two PPs: $8*A + 4*A$ (only 1 row of full adders).
 - But lots of "1"s means lots of PPs... can we improve on this?
- If we allow ourselves to subtract PPs as well as adding them (the hardware cost is virtually the same), we can re-encode arbitrarily long contiguous runs of "1" bits in the multiplier to produce just two PPs.

$$\dots 011110\dots = \dots 10000\dots - \dots 000010\dots = \dots 01000\bar{1}0\dots$$

where $\bar{1}$ indicates subtracting a PP instead of adding it. Thus we've re-encoded the multiplier using 1,0,-1 digits - aka *canonical signed digit* - greatly reducing the number of additions required.

Booth Recoding: Higher-radix mult.

 Idea: If we could use, say, 2 bits of the multiplier in generating each partial product we would **halve the number of columns and halve the latency of the multiplier!**



Booth's insight: rewrite $B_{K+1,K}^*A = 0^*A \rightarrow 0$
 $= 1^*A \rightarrow A$
 $= 2^*A \rightarrow 4A - 2A$
 $= 3^*A \rightarrow 4A - A$

2^*A and 3^*A cases, leave $4A$ for next partial product to do!

Booth recoding

On-the-fly canonical signed digit encoding!

current bit pair \swarrow \nwarrow from previous bit pair

B_{K+1}	B_K	B_{K-1}	action	
0	0	0	add 0	
0	0	1	add A	
0	1	0	add A	
0	1	1	add 2^*A	
1	0	0	sub 2^*A	
1	0	1	sub A	$\leftarrow -2^*A+A$
1	1	0	sub A	
1	1	1	add 0	$\leftarrow -A+A$

A "1" in this bit means the previous stage needed to add 4^*A . Since this stage is shifted by 2 bits with respect to the previous stage, adding 4^*A in the previous stage is like adding A in this stage!

Summary

- Performance of arithmetic blocks dictate the performance of a digital system
- Architectural and logic transformations can enable significant speed up (e.g., adder delay from $\mathcal{O}(N)$ to $\mathcal{O}(\log_2(N))$)
- Similar concepts and formulation can be applied at the system level
- **Timing analysis is tricky:** watch out for false paths!
- Area-Delay trade-offs (serial vs. parallel implementations)

Lab 4 Car Alarm - Design Approach

- Read lab/specifications carefully, use reasonable interpretation
- Use modular design - don't put everything into labkit.v
- Design the FSM!
 - Define the inputs
 - Define the outputs
 - Transition rules
- Logical modules:
 - fsm.v
 - timer.v // the hardest module!!
 - siren.v
 - fuel_pump.v
- Run simulation on each module!
- Use hex display: show state and time
- Use logic analyzer in Vivado

Car Alarm - Inputs & Outputs


 


Figure 1: System diagram showing sensors (inputs) and actuators (outputs)

Car Alarm - CMOS Implementation

 

- Design Specs
 - Operating voltage 8-18VDC
 - Operating temp: -40C +65C
 - Attitude: sea level
 - Shock/Vibration
- Notes
 - Protected against 24V power surges
 - CMOS implementation
 - CMOS inputs protected against 200V noise spikes
 - On state DC current <10ma
 - Include T_PASSENGER_DELAY and Fuel Pump Disable
 - System disabled (cloaked) when being serviced.

Debugging Hints - Lab 4

- Implement a warp speed debug mode for the one hz clock. This will allow for viewing signals on the logic analyzer or Modelsim without waiting for 27/25 million clock cycles. Avoids recompilations.

```

assign warp_speed = sw[6];
always @ (posedge clk) begin
    if (count == (warp_speed ? 3 : 26_999_999)) count <= 0;
    else count <= count +1;
end


assign one_hz = (count == (warp_speed ? 3 : 26_999_999)) ;
    
```

One Hz Ticks in Modelsim

To create a one hz tick, use the following in the Verilog test fixture:

```
always #5 clk=!clk;
always begin
  #5 tick = 1;
  #10 tick = 0;
  #15;
end

 initial begin
  // Initialize Inputs
  clk = 0;
  tick = 0; ...
```



For Loops, Repeat Loops in Simulation


```
integer i; // index must be declared as integer
integer irepeat;
```

```
// this will just wait 10ns, repeated 32x.
// simulation only! Cannot implement #10 in hardware!
irepeat = 0;
repeat(32) begin
  #10;
  irepeat = irepeat + 1;
end
```

```
// this will wait #10ns before incrementing the for loop
for (i=0; i<16; i=i+1) begin
  #10; // wait #10 before increment.
  @(posedge clk);
  // add to index on posedge
end
```

```
// other loops: forever, while
```

Edge Detection

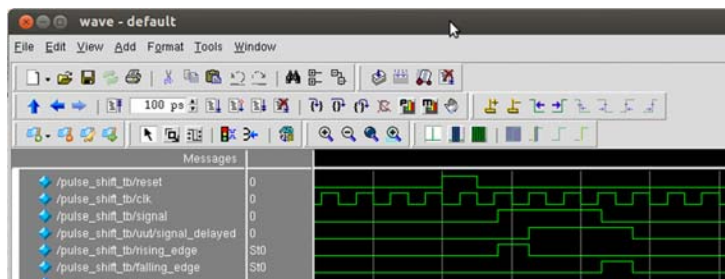

```
reg signal_delayed;

always @(posedge clk)
  signal_delayed <= signal;

assign rising_edge = signal && !signal_delayed;
assign falling_edge = !signal && signal_delayed;
```

Student Comments

- "All very reasonable except for lab 4, Car Alarm. Total pain in the ass."
- "The labs were incredibly useful, interesting, and helpful for learning. Lab 4 (car alarm) is long and difficult, but overall the labs are not unreasonable."