

MASSACHUSETTS INSTITUTE OF TECHNOLOGY
ESG Physics

8.02 with Kai

Spring 2003

Problem Set 4 Solution

Problem 1: 26.10


A variable air capacitor used in tuning circuits is made of N semicircular plates each of radius R and positioned a distance d from each other. As shown in Figure P26.10, a second identical set of plates is enmeshed with its plates halfway between those of the first set. The second set can rotate as a unit. Determine the capacitance as a function of the angle of rotation θ , where $\theta = 0$ corresponds to the maximum capacitance.

Solution:

When $\theta = \pi$, the plates are out of touch and the overlap area is zero.

When $\theta = 0$, the overlap area is that of a semi-circle $\frac{\pi R^2}{2}$.

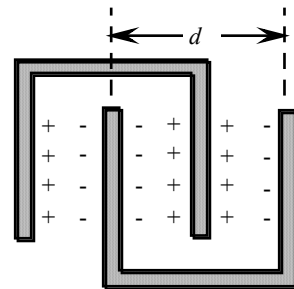By proportion, the effective area of a single sheet of charge is $\frac{(\pi - \theta)R^2}{2}$.



Where there are two plates in each comb, the number of adjoining sheets of positive and negative charge is 3, as shown in the sketch. When there are N plates on each comb, the number of parallel capacitors is and the total capacitance is


$$C = (2N - 1) \frac{\epsilon_0 A_{\text{effective}}}{r} = (2N - 1) \frac{\epsilon_0 (\pi - \theta) \frac{R^2}{2}}{\left(\frac{d}{2}\right)} \quad (1.1)$$

which gives


$$\boxed{C = \frac{(2N - 1) \epsilon_0 (\pi - \theta) R^2}{d}} \quad (1.2)$$

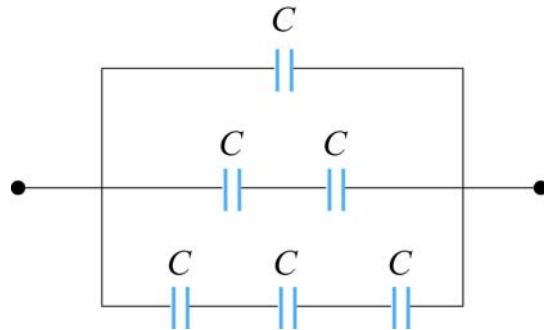Problem 2: 26.22

Evaluate the equivalent capacitance of the configuration shown in Figure P26.22. All the capacitors are identical, and each has capacitance C .



Solution:

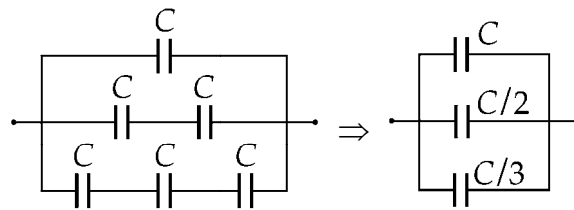

The circuit reduces first according to the rule for capacitors in series, as shown in the figure, then according to the rule for capacitors in parallel, $C_{eq} = C \left(1 + \frac{1}{2} + \frac{1}{3} \right)$


Which gives

$$\boxed{C_{eq} = 1.83 C} \quad (2.1)$$

Problem 3: 26.25

The circuit below consists of two identical parallel metallic plates connected by identical metallic springs to a battery with emf V . With the switch open, the plates are uncharged, are separated by a distance d , and have a capacitance C . When the switch is closed, the distance between the plates decreases by a factor of 0.500.

- (a) How much charge collects on each plate and
 (b) What is the spring constant for each spring? (hint: use the result of Problem 35)

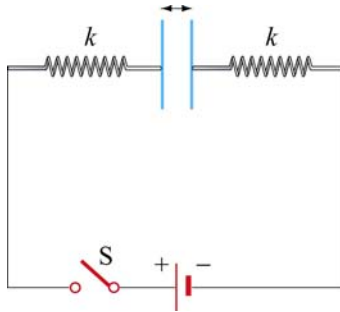**Solution:**

- (a) With the switch closed, the distance $d' = 0.500d$ and capacitance

$$C' = \frac{\epsilon_0 A}{d'} = \frac{\epsilon_0 A}{\left(\frac{d}{2}\right)} = 2C \quad (3.1)$$

therefore

$$Q = C'(\Delta V) = \boxed{2C(\Delta V)} \quad (3.2)$$

- (b) From problem 35, we know that the force exerted on each plate by the other is

$$F = \frac{Q^2}{2\epsilon_0 A} \quad (3.3)$$

Substitute the value that we get from equation (3.1), we have

$$F = \frac{Q^2}{2\epsilon_0 A} = \frac{(2CV)^2}{2\epsilon_0 A} = \frac{2C^2(\Delta V)^2}{\left(\frac{\epsilon_0 A}{d}\right)d} = \frac{2C(\Delta V)^2}{d} \quad (3.4)$$

Since one spring stretches by a distance $x = \frac{d}{4}$, we have

$$F = kx = k \frac{d}{4} = \frac{2C(\Delta V)^2}{d} \quad (3.5)$$

which gives

$$\boxed{k = \frac{8C(\Delta V)^2}{d^2}} \quad (3.6)$$


Problem 4: 26.30

Find the equivalent capacitance between points a and b in the combination of capacitors shown in Figure P26.30

Solution:

$$C_s = \frac{1}{\frac{1}{5.00} + \frac{1}{7.00}} = 2.92 \mu\text{F} \quad (4.1)$$

$$C_p = 2.92 + 4.00 + 6.00 = \boxed{12.9 \mu\text{F}} \quad (4.2)$$

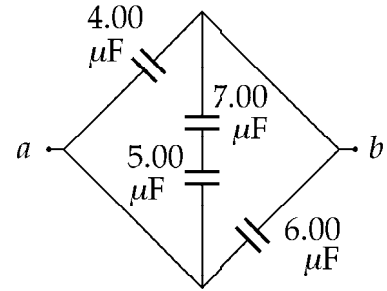

Problem 5: 26.36

Plate a of a parallel-plate, air filled capacitor is connected to a spring having force constant k , and plate b is fixed. They rest on a table top as shown (top view) in Figure P26.36. If a charge $+Q$ is placed on plate a and a charge $-Q$ is placed on plate b , by how much does the spring expand?

Solution:

Denote F_s to be the spring force and F_e to be the electric force that plate a experience, thus

$$F_s = -kx \vec{\mathbf{i}} \quad (5.1)$$

and

$$F_e = QE \vec{\mathbf{i}} \quad (5.2)$$

The electric force is due to the electric field created by plate b according to the equation

$$E = \frac{\sigma}{2\epsilon_0} = \frac{Q}{2A\epsilon_0} \quad (5.3)$$

where A is the area of one plate. Therefore

$$kx = Q \frac{Q}{2A\epsilon_0} \quad (5.4)$$

which gives

$$\boxed{x = \frac{Q^2}{2A\epsilon_0 k}} \quad (5.5)$$

Problem 6: 26.47

A conducting spherical shell has inner radius a and outer radius c . The space between these two surfaces is filled with a dielectric for which the dielectric constant is κ_1 between a and b , and κ_2 between b and c (Fig. P26.47). Determine the capacitance of this system.

Solution:

We can consider this as capacitance in series. Therefore

$$\frac{1}{C_{eq}} = \frac{1}{\left(\frac{\kappa_1 ab}{k_e (b-a)}\right)} + \frac{1}{\left(\frac{\kappa_2 bc}{k_e (c-b)}\right)} = k_e \frac{(b-a)(\kappa_2 c) + (c-b)(\kappa_1 a)}{\kappa_1 \kappa_2 abc} \quad (6.1)$$


Therefore

$$\boxed{C_{eq} = \frac{1}{k_e} \frac{\kappa_1 \kappa_2 abc}{\kappa_2 (bc - ac) + \kappa_1 (ac - ab)}} \quad (6.2)$$

Problem 7: 26.54

For the system of capacitors shown in Figure P26.54, find

- the equivalent capacitance of the system,
- the charge on each capacitor,
- the potential difference across each capacitor, and
- the total energy stored by the group

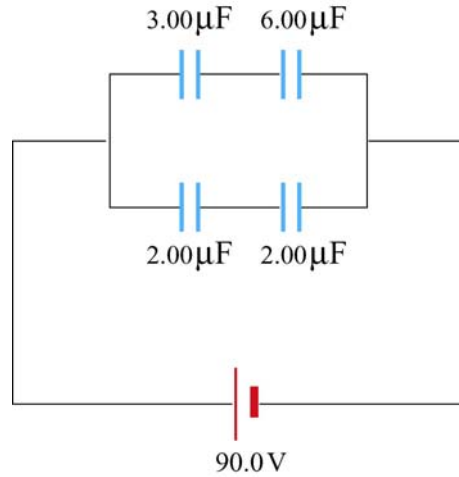**Solution:**


- (a) The equivalence capacitance is

$$C = \frac{1}{\frac{1}{3.00} + \frac{1}{6.00}} + \frac{1}{\frac{1}{2.00} + \frac{1}{4.00}} \quad (6.3)$$

which gives

$$C = 3.33 \mu\text{F} \quad (6.4)$$

- (b)

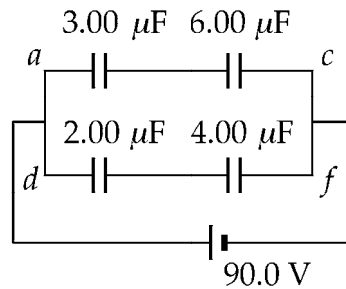

$$Q_{ac} = C_{ac} (\Delta V_{ac}) = (2.00 \mu\text{F})(90.0 \text{ V}) = 180 \mu\text{C} \quad (6.5)$$

Therefore

$$Q_3 = Q_6 = 180 \mu\text{C} \quad (6.6)$$

Similarly,

$$Q_{df} = C_{df} (\Delta V_{df}) = (1.33 \mu\text{F})(90.0 \text{ V}) = 120 \mu\text{C} \quad (6.7)$$

Therefore

$$\boxed{Q_2 = Q_4 = 120 \mu\text{C}} \quad (6.8)$$

(c)

Capacitance (C)	Charge (Q)	Potential Difference $\left(\Delta V = \frac{Q}{C}\right)$
3.00 μF	180 μC	60.0 V
6.00 μF	180 μC	30.0 V
2.00 μF	120 μC	60.0 V
4.00 μF	120 μC	30.0 V

(d)


$$U_T = \frac{1}{2} C_{eq} (\Delta V)^2 = \frac{1}{2} (3.33 \times 10^{-6}) (90.0)^2 \quad (6.9)$$

which gives

$$\boxed{U_T = 13.4 \mu\text{J}} \quad (6.10)$$

Problem 8: 26.71

A vertical parallel-plate capacitor is half filled with a dielectric for which the dielectric constant is κ . When this capacitor is positioned horizontally, what fraction of it should be filled with the same dielectric so that the two capacitors have equal capacitance?

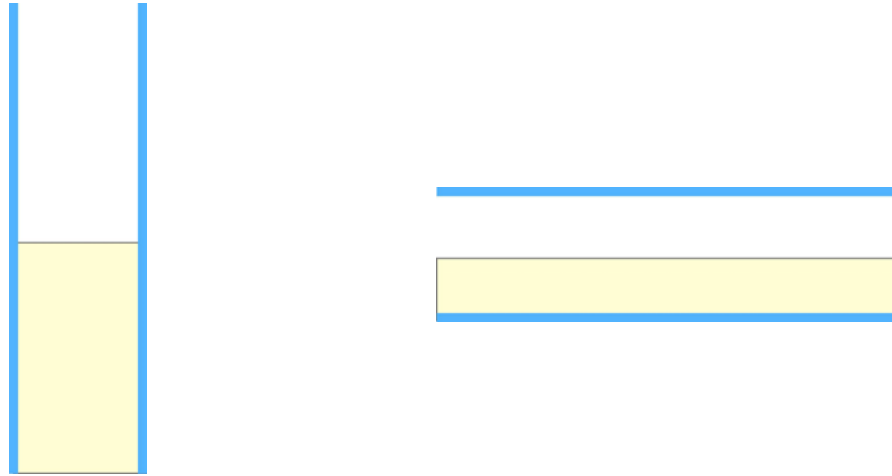**Solution:**

The vertical orientation sets up two capacitors in parallel, with equivalent capacitance

$$C_p = \frac{\epsilon_0 \left(\frac{A}{2}\right)}{d} + \frac{\kappa \epsilon_0 \left(\frac{A}{2}\right)}{d} = \frac{\kappa + 1}{2} \frac{\epsilon_0 A}{d} \quad (6.11)$$

where A is the area of either plate and d is the separation of the plates. The horizontal orientation produces two capacitors in series. If f is the fraction of the horizontal capacitor filled with dielectric, the equivalent capacitance is

$$\frac{1}{C_s} = \frac{fd}{\kappa \epsilon_0 A} + \frac{(1-f)d}{\epsilon_0 A} = \frac{f + \kappa(1-f)}{\kappa} \frac{d}{\epsilon_0 A} \quad (6.12)$$

which gives

$$C_s = \frac{\kappa}{f + \kappa(1-f)} \frac{\epsilon_0 A}{d} \quad (6.13)$$

Requiring that $C_p = C_s$, we have

$$\frac{\kappa + 1}{2} = \frac{\kappa}{f + \kappa(1-f)} \quad (6.14)$$

which gives

$$\boxed{f = \frac{\kappa - \kappa^2}{1 - \kappa^2} = \frac{\kappa}{1 + \kappa}} \quad (6.15)$$