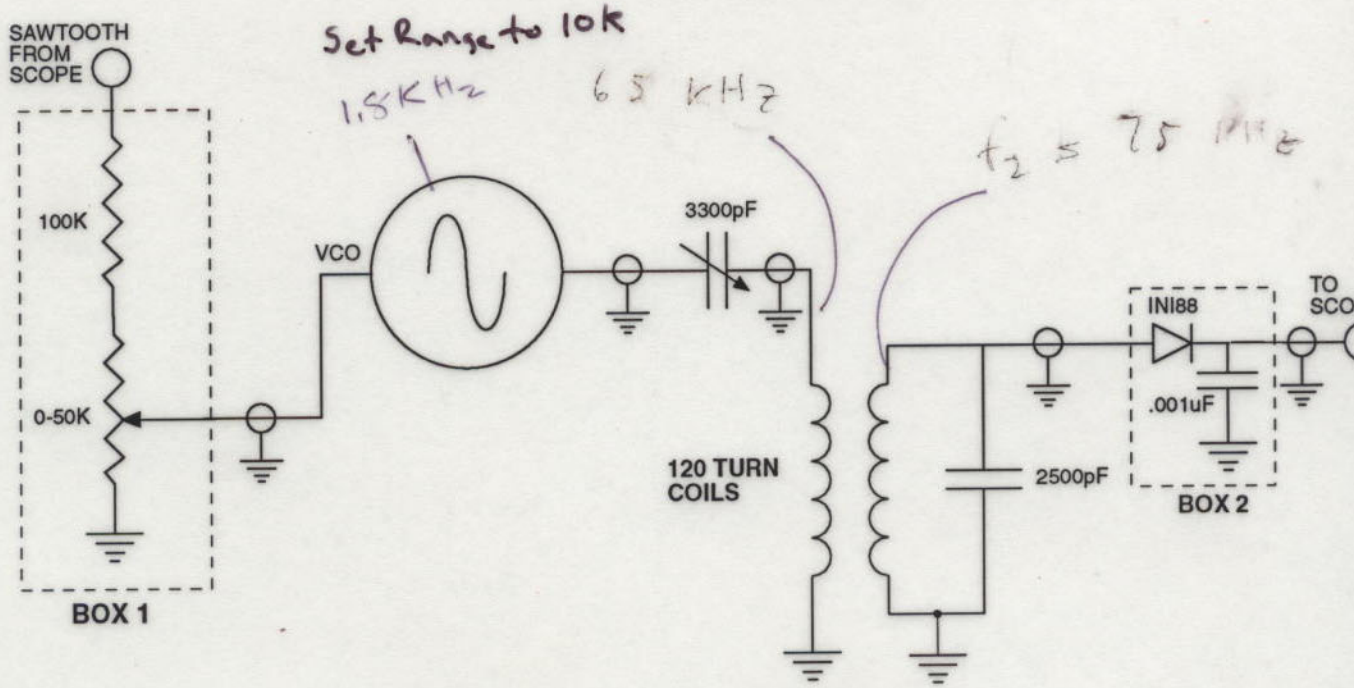


# L5

## MUTUAL INDUCTANCE WITH TWO COILS RESONANT

# L




L5

# MUTUAL INDUCTANCE WITH TWO COILS RESONANT




L5
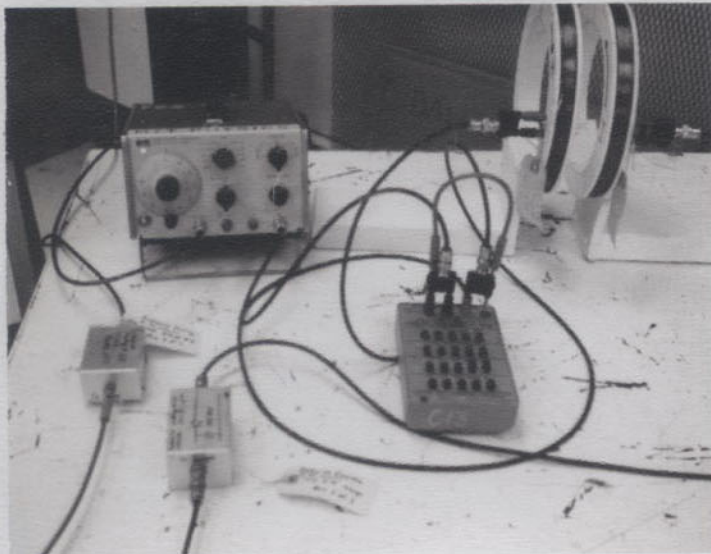
## LC & RLC CIRCUITS - Resonance

Two 120-turn coils are placed facing each other on the lectrue table. Each of the coils are series with a capacitor, the values of which have been chosen such that the two LC circuits have slightly different resonant frequencies. One of the coils is driven by a sine wave generator, whose output is swept over a frequency range encomapssing the resonant frequency of both LC circuits. When the voltage across the capacitor of the secondary coil is displayed on an oscilloscope, a double resonance curve caused by the resonance in ea coil is observed.




Range = 10K

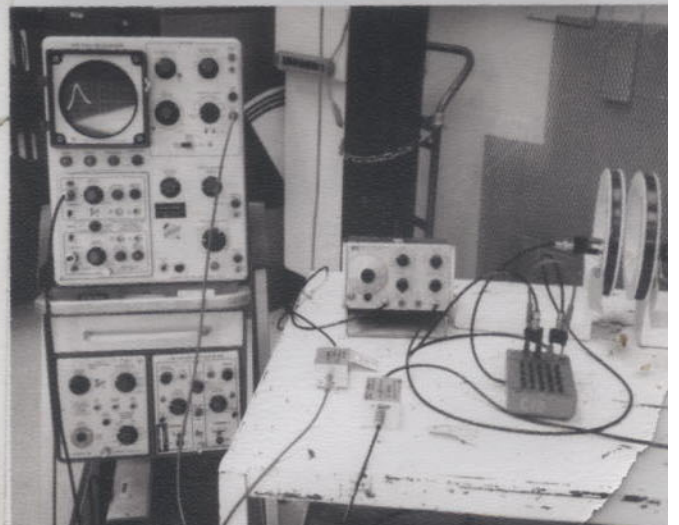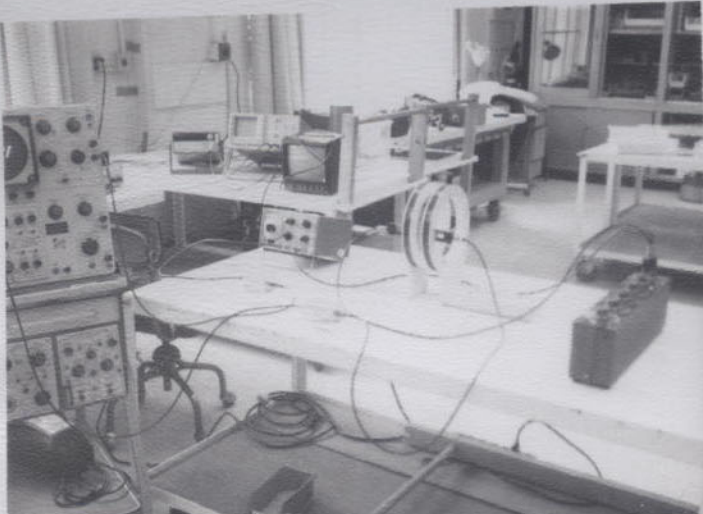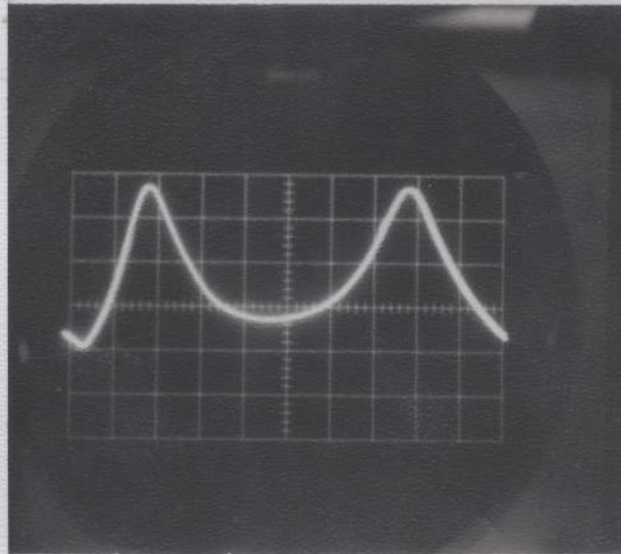

# MUTUAL INDUCTANCE W/TWO COILS RESONANT
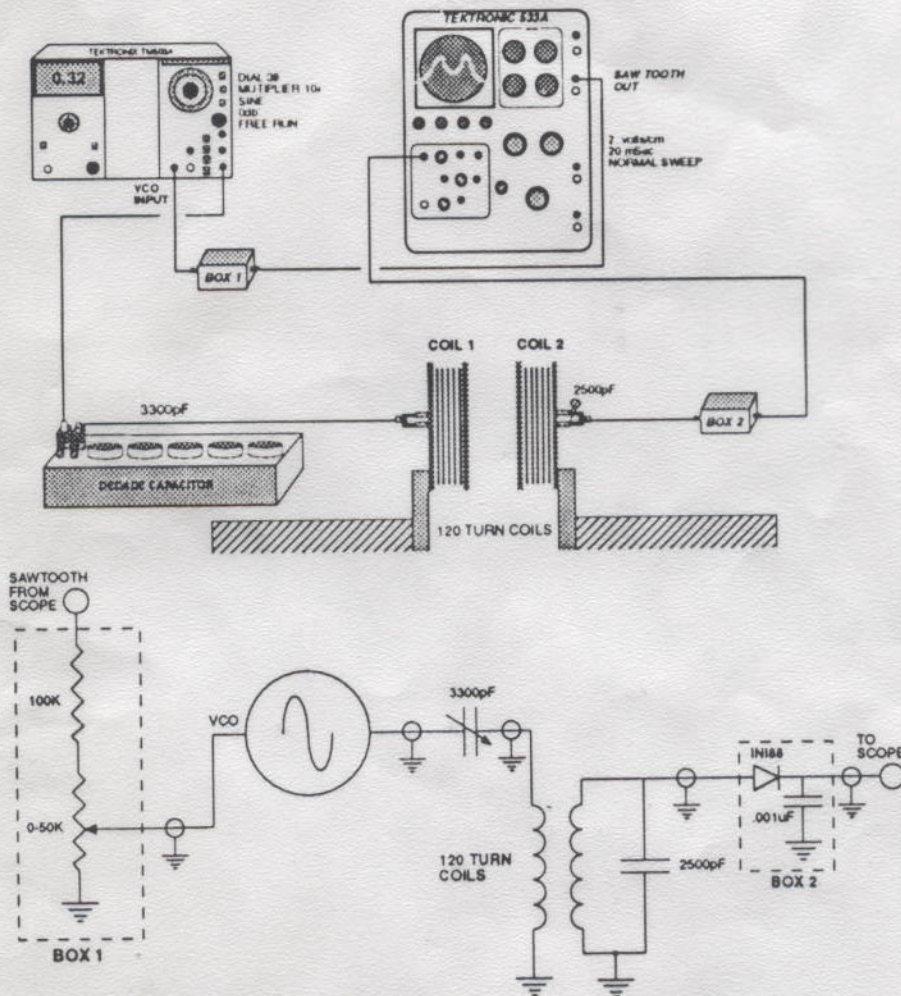
## RESONANCE- LC Resonance

Two 120-turn coils are placed facing each other on the lecture table. Each of the coils is in series with a capacitor, the values of which have been chosen such that the two LC circuits have slightly different resonant frequencies. One of the coils is driven by a sine wave generator, whose output swept over a frequency range encompassing the resonant frequency of both LC circuits. When the voltage across the capacitor of the secondary coil is displayed on an oscilloscope, a resonant curve caused by the resonance in each coil is observed.



RESONANT FREQUENCY:  $f = \frac{1}{2\pi} \left( \frac{1}{\sqrt{LC}} \right)$

1st circuit (coil)  $L = 5 \times 10^{-3} \text{ H}$   $C = 3300 \text{ pF}$   $f = 39 \text{ kHz}$

2nd circuit (coil)  $L = 5 \times 10^{-3} \text{ H}$   $C = 2500 \text{ pF}$   $f = 45 \text{ kHz}$


L5

## MUTUAL INDUCTANCE WITH TWO COILS RESONANT




L5
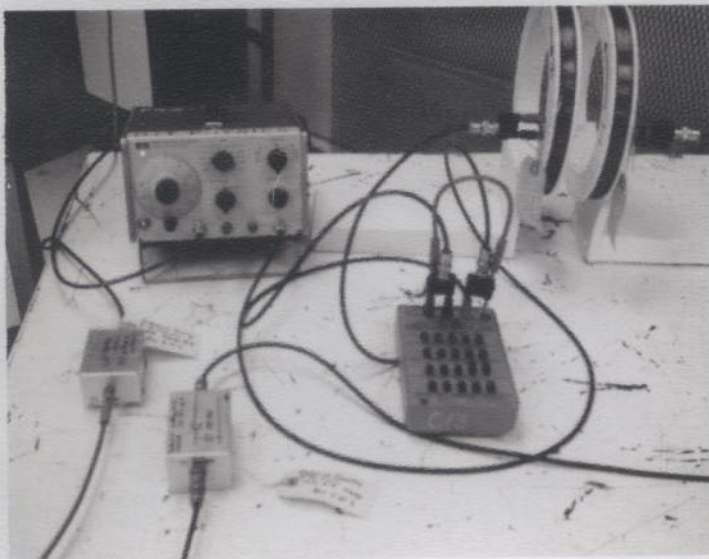
### LC & RLC CIRCUITS - Resonance

Two 120-turn coils are placed facing each other on the lectrue table. Each of the coils are series with a capacitor, the values of which have been chosen such that the two LC circuit have slightly different resonant frequencies. One of the coils is driven by a sine wave generator, whose output is swept over a frequency range encomapssing the resonant frequency of both LC circuits. When the voltage across the capacitor of the secondary coil is displayed on an oscilloscope, a double resonance curve caused by the resonance in ea coil is observed.



Range = 10K

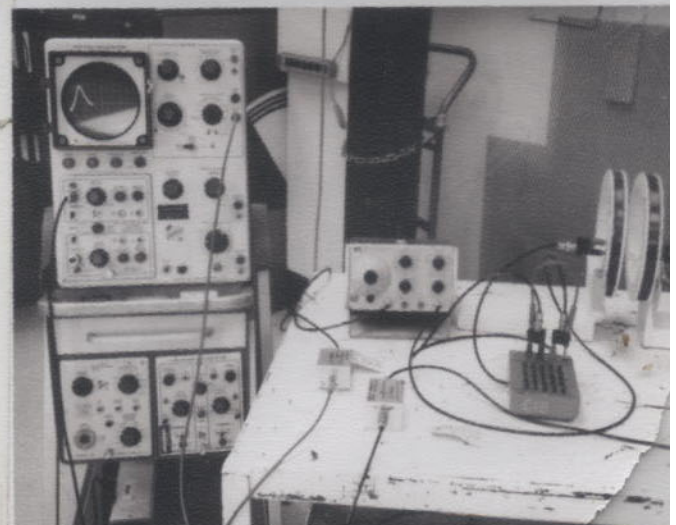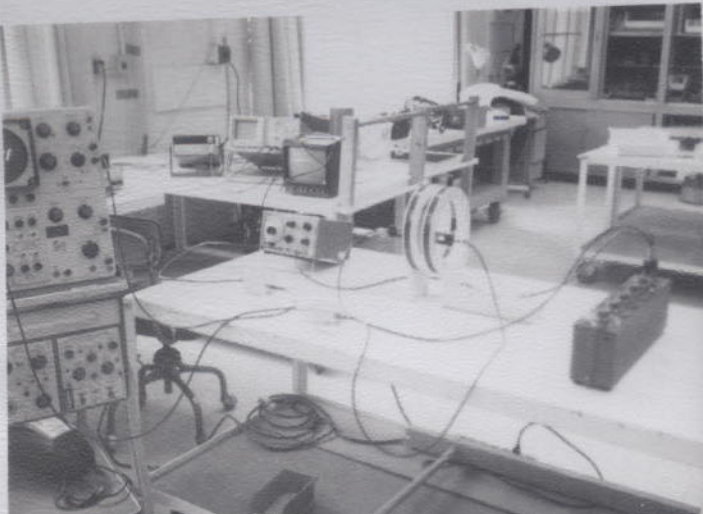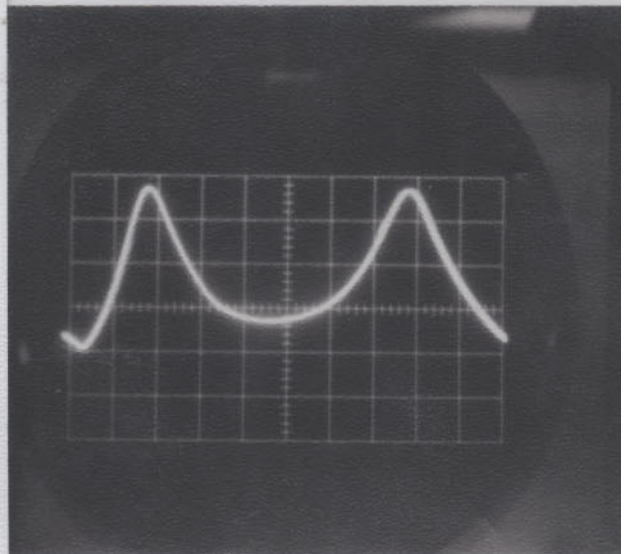


L5


# MUTUAL INDUCTANCE W/TWO COILS RESONANT

L

RESONANCE-LC Resonance

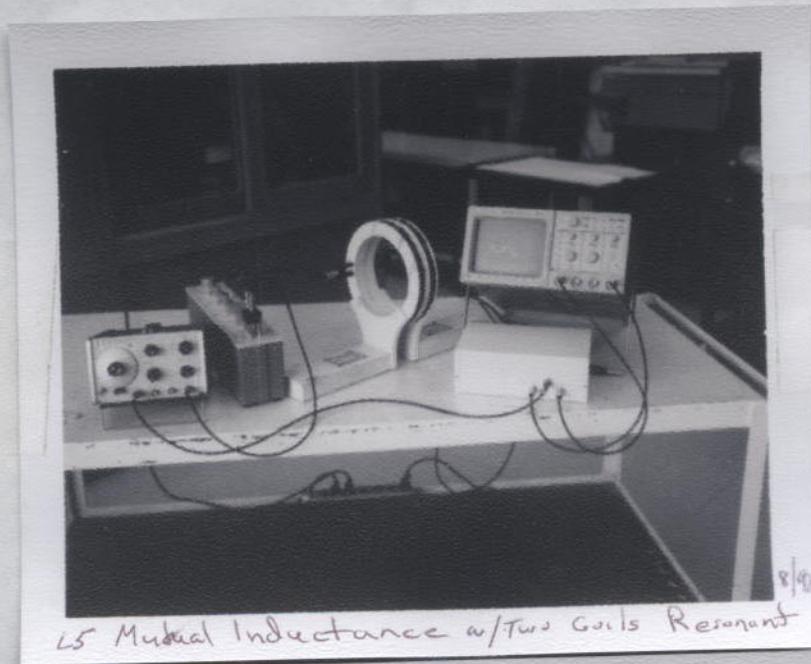

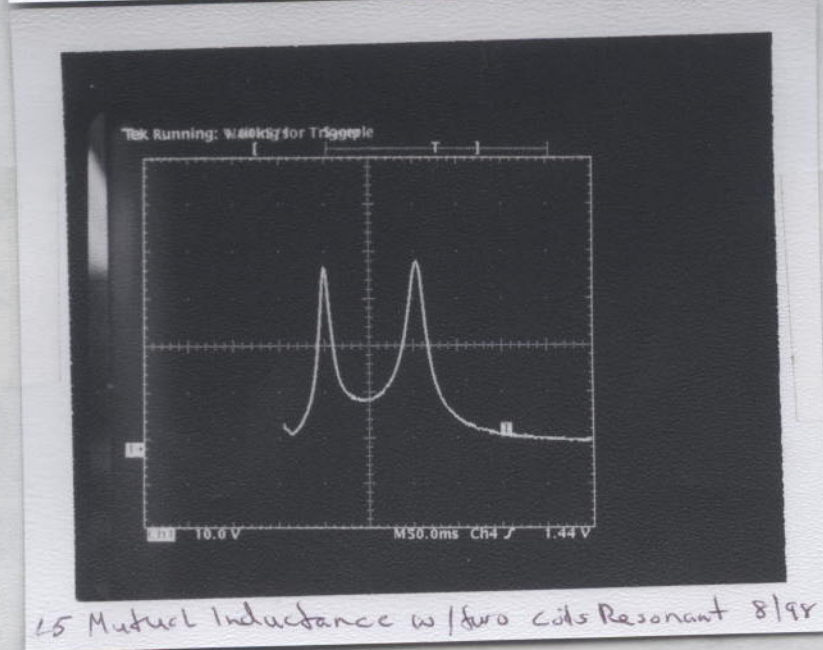L5 Mutual Inductance w/Two Coils Resonant



L5 Mutual Inductance w/Two Coils Resonant 8/98

# L5

## MUTUAL INDUCTANCE W/TWO COILS RESONANT

# L5

### RESONANCE-LC Resonance

#### Parts List:

- Tektronix 533 scope
- HP 3310A function generator
- GenRad decade capacitor
- two miniboxes labeled "inductive coupling of LC circuits"
- 4- male banana to female BNC connector
- 5- BNC cables
- 2 -120 turn coils
- 2500pF capacitor

#### Setup:

1. Connect the 2500pF cap across the terminals of one of the coils
2. Attach the banana to BNC adaptor to each of the coils terminal pairs
3. Connect one banana to BNC adaptor between High and GND of the decade capacitor.
4. Wire the rest of the circuit according to schematic.
5. Set the decade capacitor to 3300pF.
6. Set the function generator to  $\approx 38\text{KHZ}$ . *Important: Range = 10K at 3-4*
7. Set the scope to 10 msec/div., internal trigger, 1 v/cm vertical, DC coupled.

NOTE: adjustment of resistor in Box 1 might be necessary.

#### Operation:

Adjust both coils until the peaks of each resonant point are equal. By varying the coupling between the two coils, one can show that both amplitude and frequency are varied.