

Free 1977

## APPLICATION LITERATURE NUMERICAL LIST

APPLICATION NOTES		DATE
AN-1	A Versatile Monolithic Voltage Regulator . . . . .	11/67
AN-2	Designing Switching Regulators . . . . .	3/69
AN-3	Drift Compensation Techniques for Integrated DC Amplifiers . . . . .	11/67
AN-4	Monolithic Op Amp - The Universal Linear Component . . . . .	4/68
AN-5	A Fast Integrated Voltage Follower with Low Input Current . . . . .	5/68
AN-6	Tuned Circuit Design Using Monolithic RF/IF Amplifiers . . . . .	3/68
AN-8	New Uses for the LM100 Regulator . . . . .	6/68
AN-10	Low Power Operational NH0001 Amplifier . . . . .	12/68
AN-13	NH0002 Current Amplifier . . . . .	9/68
AN-15	A Complete Monolithic IF Strip for AM/AGC Applications . . . . .	8/68
AN-20	An Applications Guide for Op Amps . . . . .	2/69
AN-21	Designs for Negative Voltage Regulators . . . . .	12/68
AN-23	The LM105 - An Improved Positive Regulator . . . . .	1/69
AN-24	A Simplified Test Set for Op Amp Characterization . . . . .	6/69
AN-28	High Speed MOS Commutators . . . . .	1/70
AN-29	IC Op Amp Beats FETs on Input Current . . . . .	12/69
AN-30	Log Converters . . . . .	11/69
AN-31	Op Amp Circuit Collection . . . . .	2/70
AN-32	FET Circuit Applications . . . . .	2/70
AN-33	Analog-Signal Commutation . . . . .	2/70
AN-34	How to Bias the Monolithic JFET Dual . . . . .	3/70
AN-38	Applications of MOS Analog Switches . . . . .	5/70
AN-41	Precision IC Comparator Runs from +5V Logic Supply . . . . .	10/70
AN-42	IC Provides On-Card Regulation for Logic Circuits . . . . .	2/71
AN-46	The Phase Locked Loop IC as a Comm. System Building Block . . . . .	6/71
AN-48	Applications for a New Ultra-High Speed Buffer . . . . .	8/71
AN-49	PIN Diode Drivers . . . . .	8/71
AN-51	A Unique Monolithic AGC/Squelch Amplifier . . . . .	9/71
AN-53	High Speed Analog Switches . . . . .	9/71
AN-54	A Complete Monolithic AM/FM/SSB IF Strip . . . . .	4/72
AN-56	1.2 Volt Reference . . . . .	12/71
AN-63	New Design Techniques for FET Op Amps . . . . .	3/72
AN-64	LM381 Low Noise Dual Preamplifier . . . . .	5/72
AN-69	LM380 Power Audio Amplifier . . . . .	12/72
AN-70	LM381A Dual Preamplifier for Ultra-Low Noise Applications . . . . .	8/72
AN-71	Micropower Circuits Using the LM4250 Programmable Op Amp . . . . .	7/72
AN-72	The LM3900 - A New Current-Differencing Quad of $\pm$ Input Amplifiers . . . . .	9/72
AN-74	LM139/LM239/LM339 - A Quad of Independently Functioning Comparators . . . . .	1/73
AN-75	Applications for a High Speed FET Input Op Amp . . . . .	12/72
<b>LINEAR BRIEFS</b>		
LB-1	Instrumentation Amplifier . . . . .	3/69
LB-2	Feedforward Compensation Speeds Op Amp . . . . .	3/69
LB-3	Worst Case Power Dissipation in Linear Regulators . . . . .	4/69
LB-4	Fast Compensation Extends Power Bandwidth . . . . .	4/69
LB-5	High Q Notch Filter . . . . .	3/69
LB-6	Fast Voltage Comparators with Low Input Current . . . . .	5/69
LB-7	Tracking Voltage Regulators . . . . .	8/69
LB-8	Precision AC/DC Converters . . . . .	8/69
LB-9	Universal Balancing Techniques . . . . .	8/69
LB-10	IC Regulators Simplify Power Supply Design . . . . .	1/70
LB-11	The LM110 - An Improved IC Voltage Follower . . . . .	3/70
LB-12	An IC Voltage Comparator for High Impedance Circuitry . . . . .	1/70
LB-13	Applications of the LM173/LM273/LM373 . . . . .	11/70
LB-14	Speed Up the LM108 Feedforward Compensation . . . . .	11/70
LB-15	High Stability Regulators . . . . .	1/71
LB-16	Easily Tuned Sine Wave Oscillators . . . . .	3/71
LB-17	LM118 Op Amp Slews 70V/ $\mu$ sec . . . . .	9/71
LB-18	+5 to -15 Volts DC Converter . . . . .	7/72
LB-19	Predicting Op Amp Slew Rate Limited Response . . . . .	8/72
LB-20	A Fully Differential Input Voltage Amplifier . . . . .	12/72

TK7874

N3

C.2

V.1